
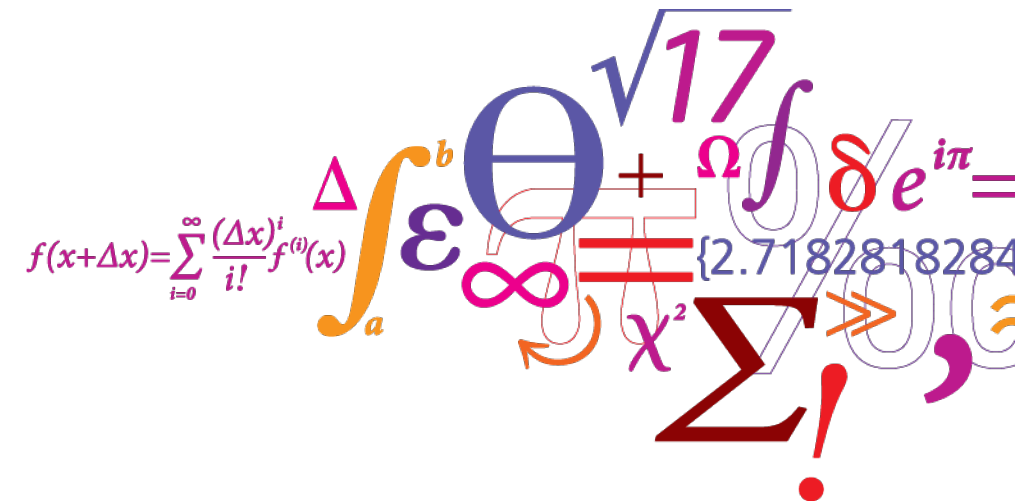


# Transmission Lines

Spyros Chatzivasileiadis

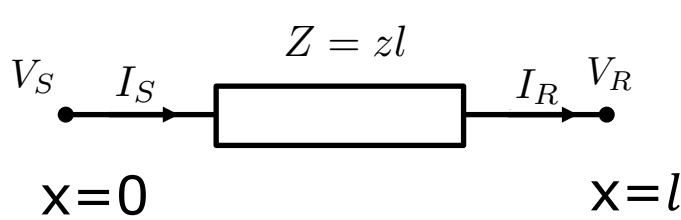


# Line Models




$$\begin{bmatrix} V_S \\ I_S \end{bmatrix} = \begin{bmatrix} 1 & Z \\ 0 & 1 \end{bmatrix} \begin{bmatrix} V_R \\ I_R \end{bmatrix}$$

**←**  
 $Y = 0$

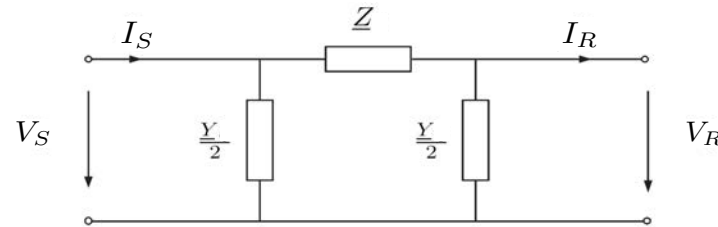


$$\begin{bmatrix} V_S \\ I_S \end{bmatrix} = \begin{bmatrix} 1 + \frac{YZ}{2} & Z \\ Y \left( 1 + \frac{YZ}{4} \right) & 1 + \frac{YZ}{2} \end{bmatrix} \begin{bmatrix} V_R \\ I_R \end{bmatrix}$$

**←**  
 $\gamma l \ll 1$

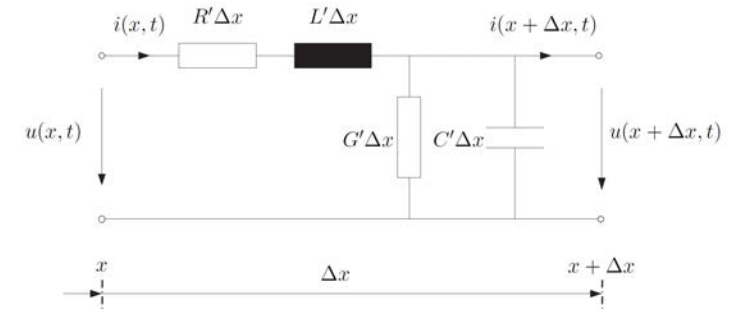

$$\begin{bmatrix} V_S \\ I_S \end{bmatrix} = \begin{bmatrix} \cosh(\gamma l) & Z_c \sinh(\gamma l) \\ \frac{1}{Z_c} \sinh(\gamma l) & \cosh(\gamma l) \end{bmatrix} \begin{bmatrix} V_R \\ I_R \end{bmatrix}$$


# Line Models

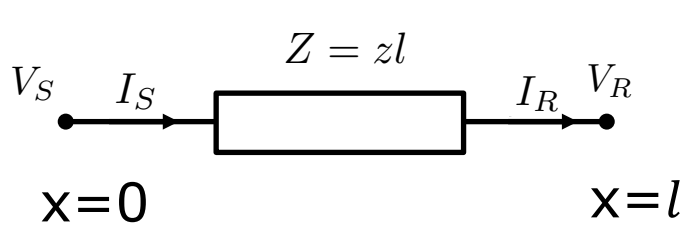

$l \leq 25 \text{ km}$

$$\begin{bmatrix} V_S \\ I_S \end{bmatrix} = \begin{bmatrix} 1 & Z \\ 0 & 1 \end{bmatrix} \begin{bmatrix} V_R \\ I_R \end{bmatrix}$$


$Y = 0$

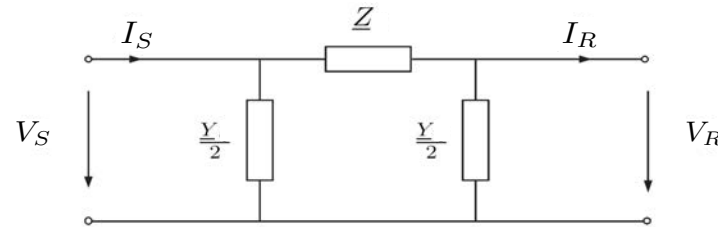

$l \leq 250 \text{ km}$

$$\begin{bmatrix} V_S \\ I_S \end{bmatrix} = \begin{bmatrix} 1 + \frac{YZ}{2} & Z \\ Y \left( 1 + \frac{YZ}{4} \right) & 1 + \frac{YZ}{2} \end{bmatrix} \begin{bmatrix} V_R \\ I_R \end{bmatrix}$$

$\gamma l \ll 1$

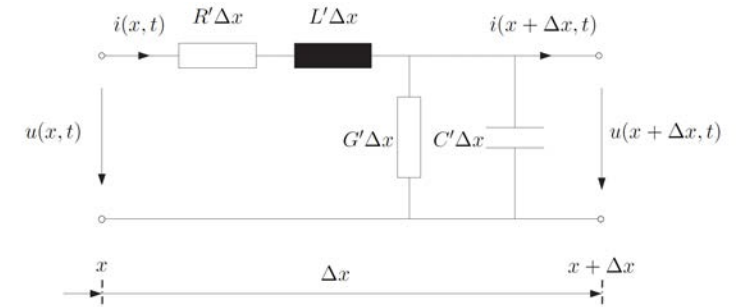

$l > 250 \text{ km}$

$$\begin{bmatrix} V_S \\ I_S \end{bmatrix} = \begin{bmatrix} \cosh(\gamma l) & Z_c \sinh(\gamma l) \\ \frac{1}{Z_c} \sinh(\gamma l) & \cosh(\gamma l) \end{bmatrix} \begin{bmatrix} V_R \\ I_R \end{bmatrix}$$

- How much is the surge impedance of a lossless line?
- What happens when we connect at the end of the line a load equal to the surge impedance of the line?


# Surge impedance loading

- How much is the surge impedance of a lossless line?
- The surge impedance of a lossless line is pure resistive

$$Z_c = \sqrt{\frac{L}{C}}$$

- At surge impedance loading the power line is in a state of **reactive power balance**
  - Series inductances consume the same amount of reactive power as the shunt capacitances produce
  - Reactive power consumed on series inductance: dependent on current through the line
  - Reactive power consumed on shunt capacitance: dependent on voltage at line ends

# Reactive power demand of a line

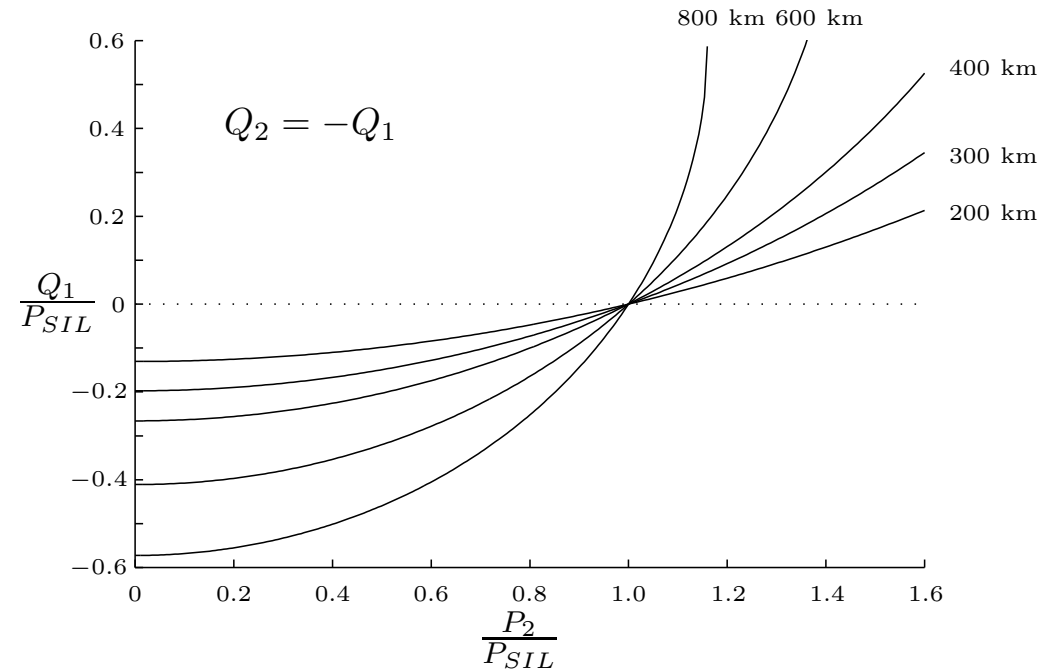

**Figure 6.3.** The reactive power demand at the beginning of the line, as a function of the active power at the end of the line ( $U_1 = U_2$ , lossless line).

Figure taken from:  
 G. Andersson and C. Franck, *Electric Power Systems, Lecture Notes, ETH Zurich, 2013*

# Voltage Profiles

**FIGURE 5.10**

Voltage profiles of an uncompensated lossless line with fixed sending-end voltage for line lengths up to a quarter wavelength

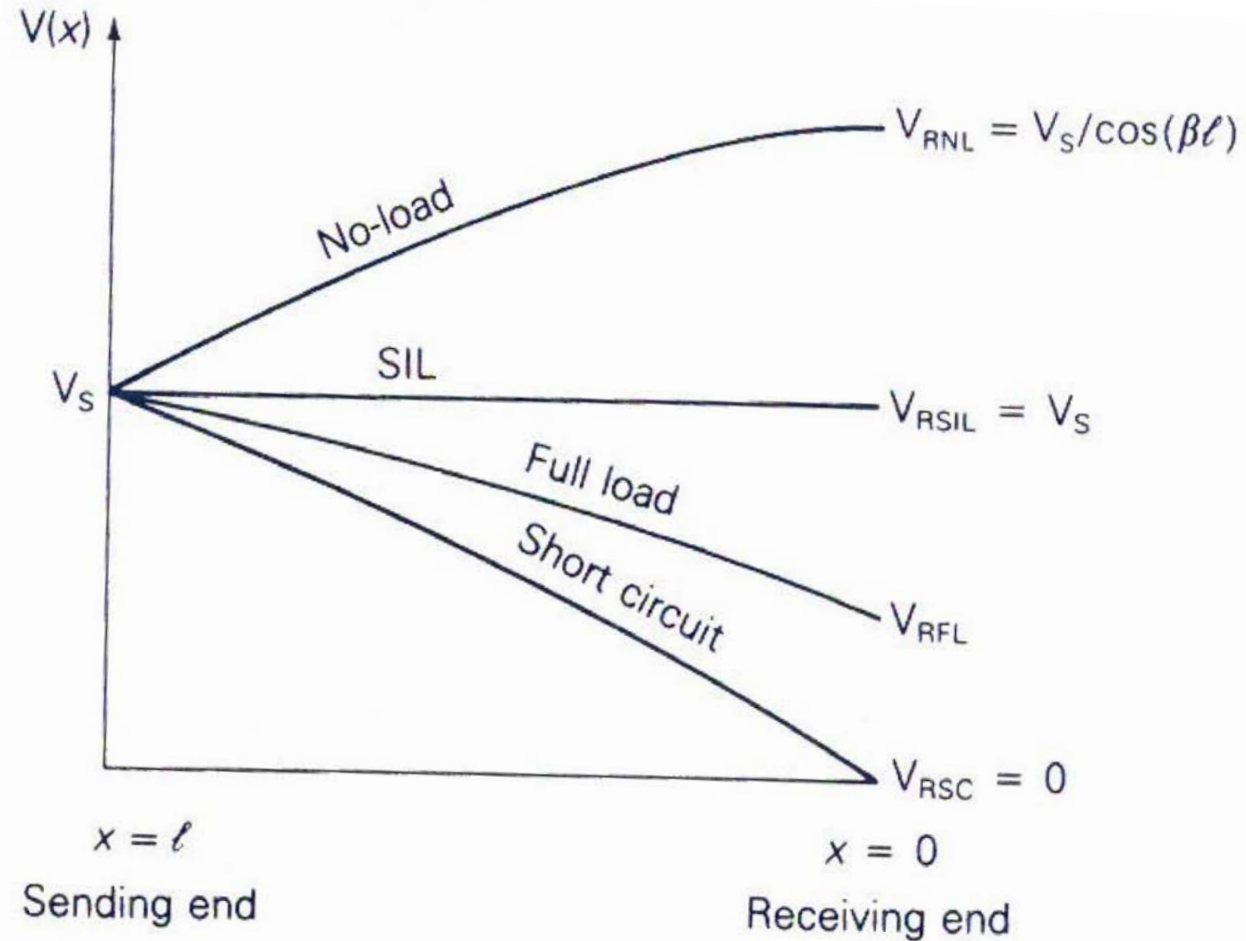


Figure taken from:  
*J. Glover, T. Overbye, M. Sarma, Power System Analysis and Design, Cengage Learning, Sixth Edition, 2016*

# Voltage at the beginning of the line for different power factors

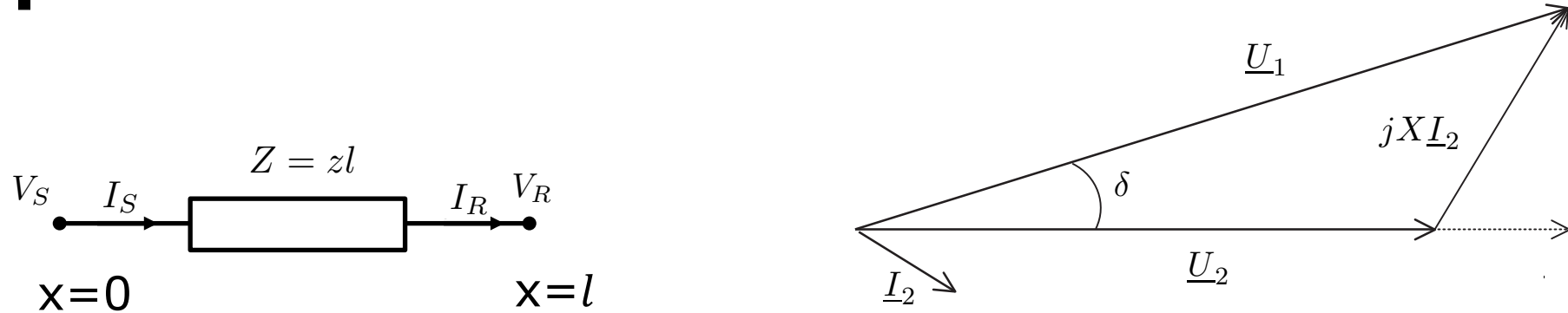
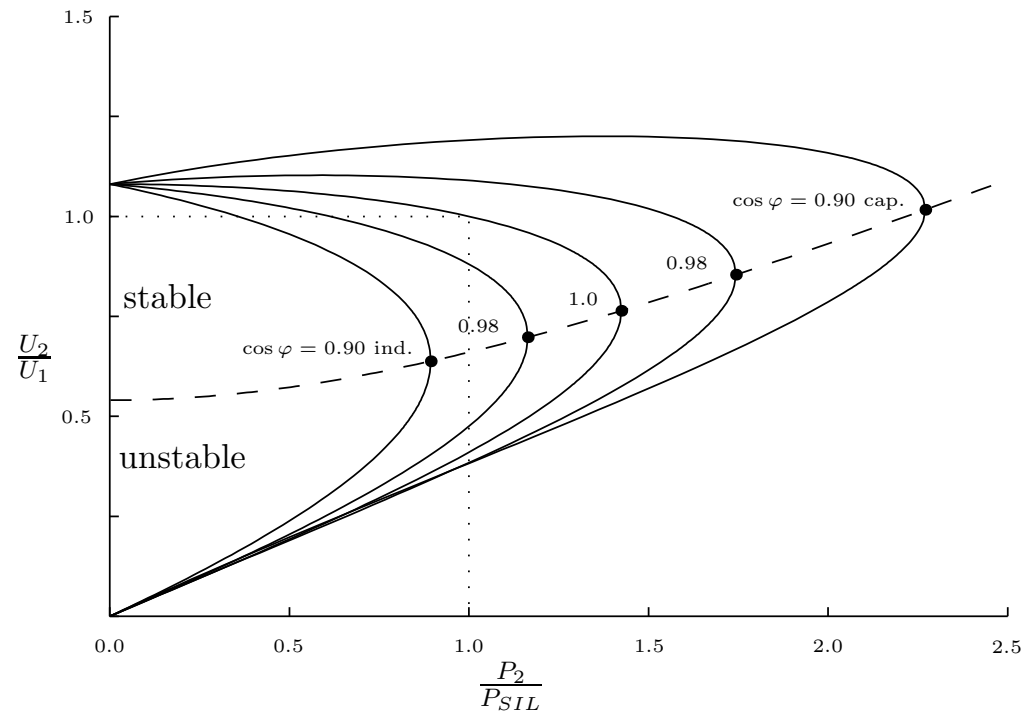


Figure 6.7. Simplified relation between the phasors  $\underline{U}_1$  and  $\underline{U}_2$ .

- The above diagram shows the voltage and current phasors for an inductive load (lagging power factor) and a line modelled as a series inductance
- Draw the phasor diagrams and describe what happens with the voltage angle and magnitude for:
  1.  $\cos\varphi = 1$
  2.  $P=P_{SIL}$  (here you must use the exact parameters/equations for the lossless lines)
  3.  $\cos\varphi$  : leading

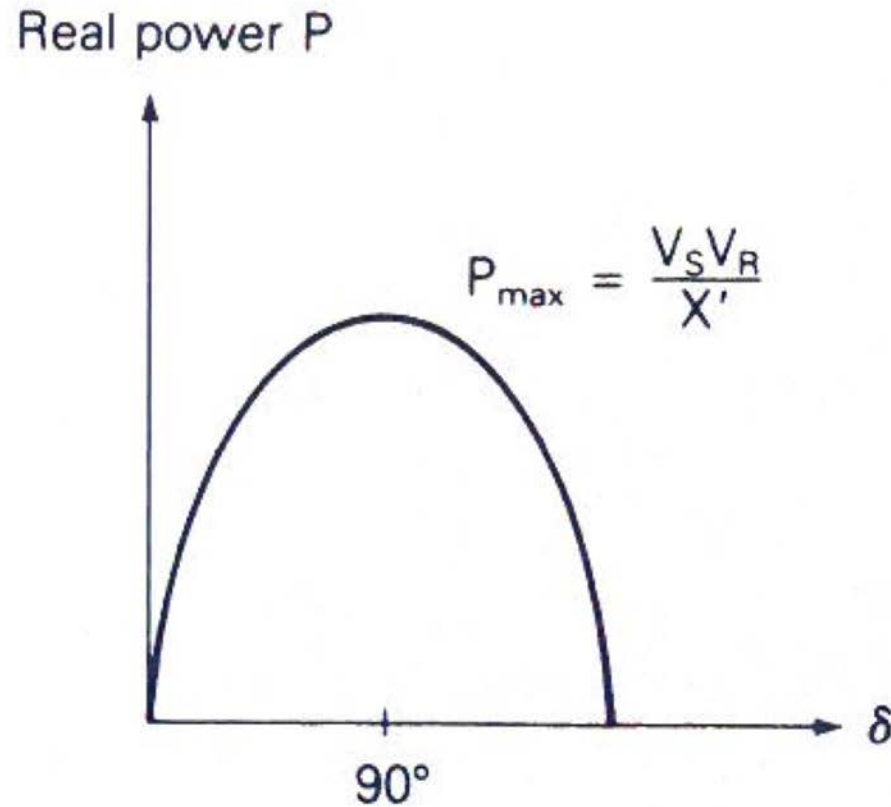




**Figure 6.10.** Voltage at the end of the line as a function of the delivered active power for different line loadings.  $U_1$  is kept constant at 1.0 pu.

Figure taken from:  
 G. Andersson and C. Franck, *Electric Power Systems, Lecture Notes, ETH Zurich, 2013*

# Steady-state stability limit



**FIGURE 5.11**

Real power delivered by a lossless line versus voltage angle across the line

# Line Loadability

**FIGURE 5.12**

Transmission-line loadability curve for 60-Hz overhead lines—no series or shunt compensation

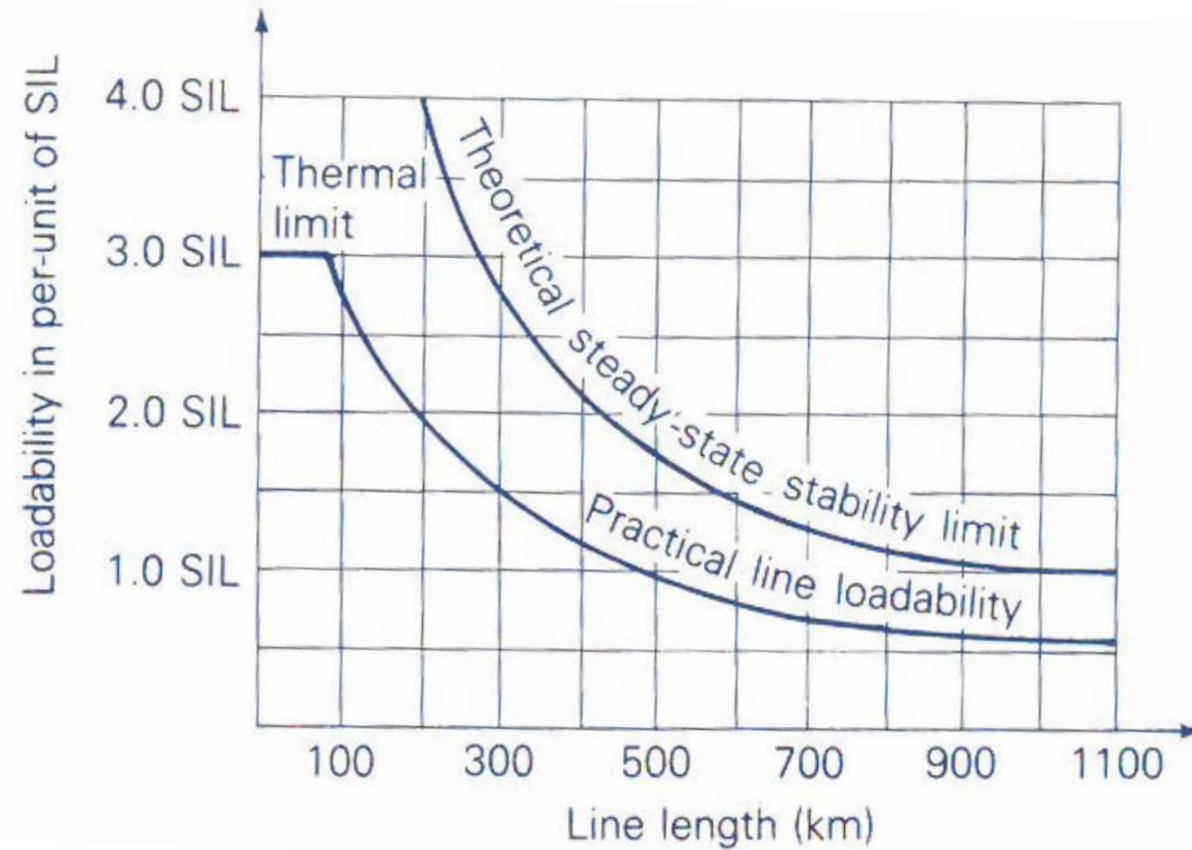


Figure taken from:  
*J. Glover, T. Overbye, M. Sarma, Power System Analysis and Design, Cengage Learning, Sixth Edition, 2016*

# Shunt Reactive Compensation

- You are given:
  1. Nominal voltage at full load conditions
  2. Current at full load conditions
- You need to determine
  - Nominal voltage at sending end
  - Percent voltage regulation at no-load conditions
  - Shunt reactive compensation to stay within limits